



Tutorial



Common Mistakes

- Didn't used \$finish at the end of testbench.
- Using initial block instead of always/forever block for clock.
- Forget to initialize clock in the testbench.
- Using incorrect module names and forgetting semicolon at the end of each line.




More About Flip Flops

Why do we need one more flip-flop?

- No Invalid States
- Need a device which can toggle its previous state.

JK-Flip Flop

$$Q(t+1) = J\bar{Q}(t) + Q\bar{K}(t)$$

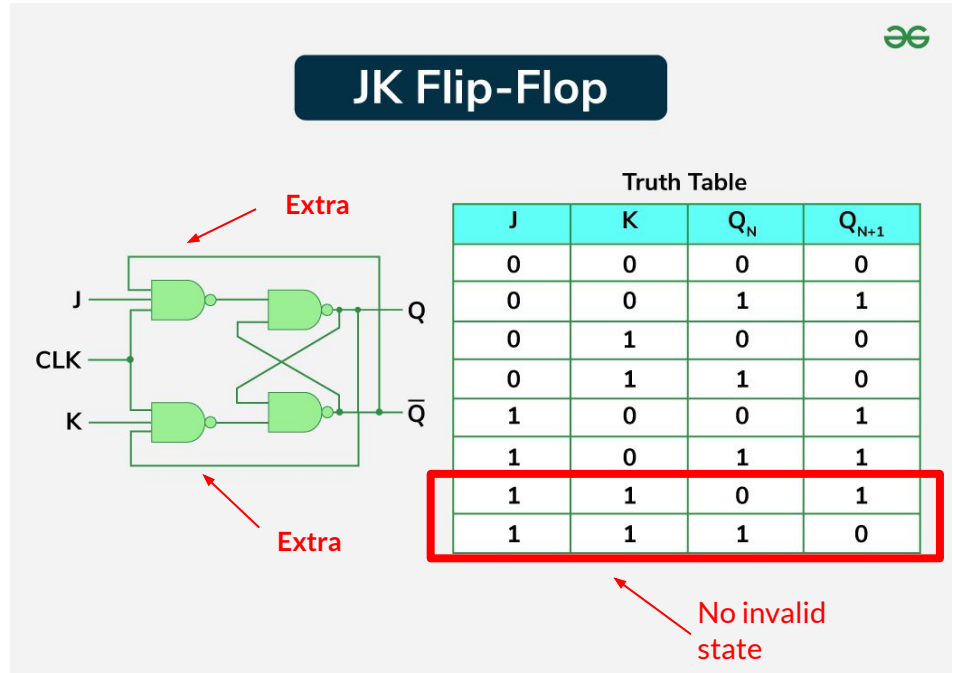



Task-1


JK Flip Flop (Behavioral) Implementation in Verilog



FSM

Task 1

Coding the given FSM in verilog

 



Task 2

The following is the state transition table for a Moore machine with one input, one output, and four states. Implement this state machine. Include a reset that resets the FSM to state A.

State	Next state		Output
	in=0	in=1	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	B	1