 


Q1]



Q3]


a) Input = ~~10010~~ 10100111
 Output = 00010101

key = Input \oplus output = 10110010

b) Key generated : 1 0 1 1

to get the first 4 key outputs as 1011, initial state needs to be: $A[3]=1$, $A[2]=1$, $A[1]=0$, $A[0]=1$

 c) We know, Initial State of Shift Register



(We don't know which bit out of $A[1]$, $A[2]$, $A[3]$ is being used to XOR)

↳ To figure out the XOR BIT we look at the next BITS of Key generated.

<u>Current State</u>	<u>Next Keybit to generate</u>	<u>XOR Options</u>	<u>Key</u>
1101	0	$A[3]$ or $A[2]$	10110010
0110	0	<u>Only $A[3]$</u>	

↳ This means XORing the $A[3]$ with $A[0]$ gives our new $A[3]$ and we may not check any further.